

14.10.26

Electrcity

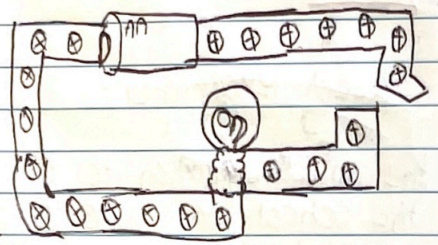

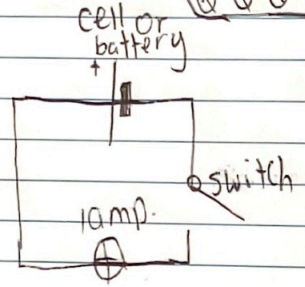

Voltage = V

(volts)(V)


Current (I)

Amps = A

Resistance = (R)

(Ohms) Ω

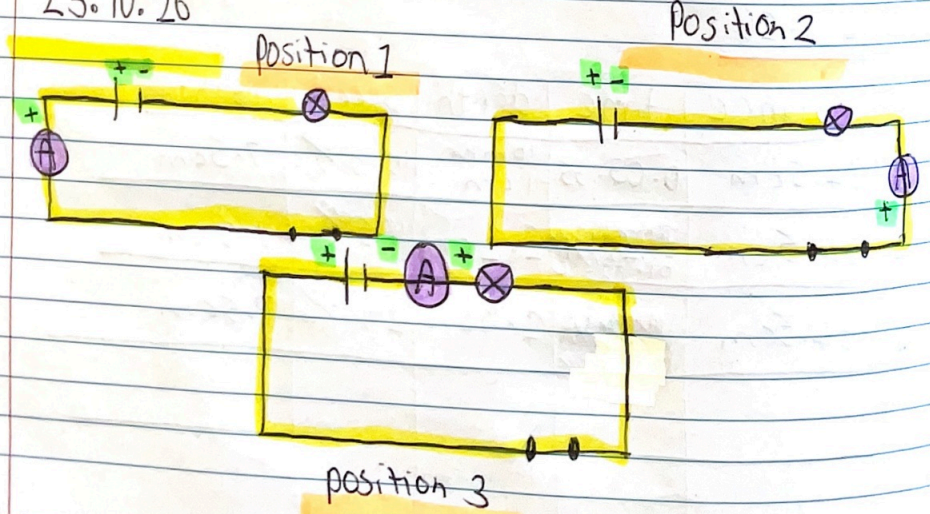23.10.26

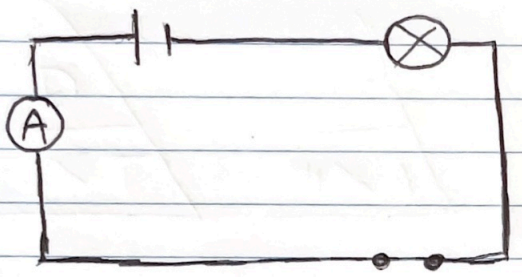


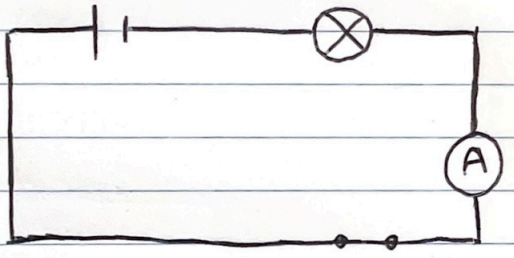
position 1
Ammeter: 2

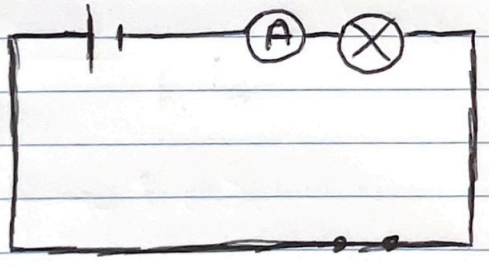
position 2
Ammeter: 2

position 3
Ammerter: 2

23/10/26

① 

② 

③ 

Prediction:

I think these three ammeter readings will be different because the current going through the wires will slow down especially after going through the lightbulb since it requires a lot of energy in order to work properly.


Results:

I was WRONG!
They were all the same!


Key Words:

* Current: The energy that keeps going
* Ammeter: Device to measure current
* Voltage: Energy
* Circuit: Connecting devices together that work as one


23/10/26 ①

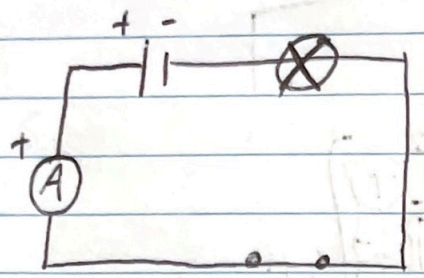

②

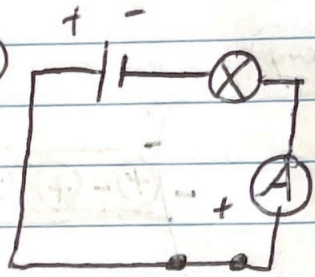

③

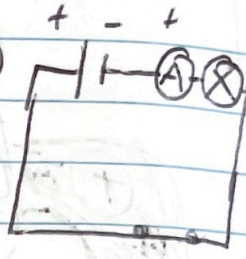

Different because the current ~~is~~ would be weaker after going through the lightbulb because the lightbulb would use up some of the energy. Put ~~to be~~ the ammeter before the lightbulb and the current will be stronger. ~~I don't ever same~~ 3.5 weaker.

① ammeter reading - ~~0.28~~ ~~29~~ 24

② ammeter reading - ~~0.28~~ 24


③ ammeter reading - ~~0.38~~ 24

Current isn't used up by the light so current stays the same everywhere charge remains constant. lightbulb uses energy.


Key words
- current (flowing charge)
- ammeter (device that measures amps current)
- voltage (how much energy that is provided to charge)
- circuit (use wires to connect different devices into something that can work)

23 Oct 2026


Position 1

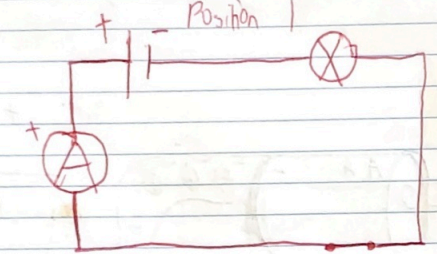

Position 2

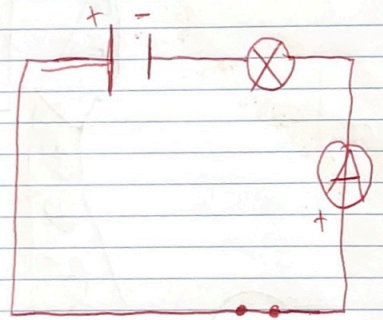

Position 3

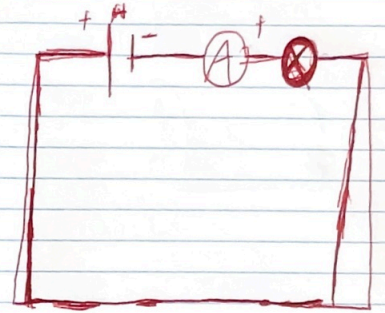

~~Amps Position 1 = 1.7 Amps~~

Prediction: My prediction is that it'll be the same ~~as~~

Position 1 = 1.7 Amps


Position 2 = 1.6 Amps

Position 3 = 1.6 Amps

	distance	time	depth	speed	hight
1	34.5cm	03.35sec	1cm	10.3 cm/sec	7.5cm
2	34.5cm	01.87sec	2.2cm	18.5 cm/sec	7.5cm
3	34.5cm	01.25sec	2.8cm	27.6 cm/sec	7.5cm

23.10.26

prediction and retrieval

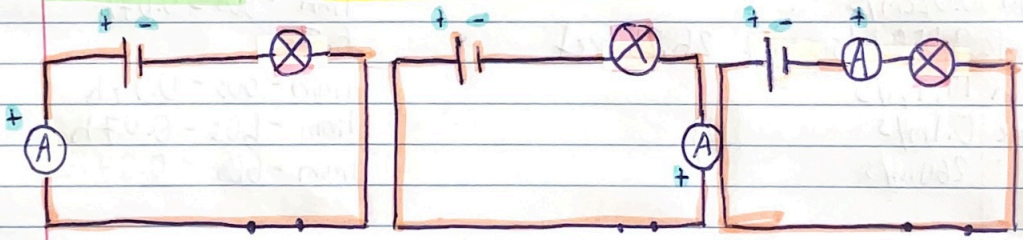

position 1 | position 2 | position 3

Ammeter: 2 | Ammeter: 2 | Ammeter: 2

Key words:

- current
- ammeter
- voltage
- circuit