Voltage and current investigation

Name [redacted] Class _____ Date 28.10.26

How does changing voltage affect current?

My prediction

I think
that not to much will happen.

because
last time nothing really happened.

Circuit

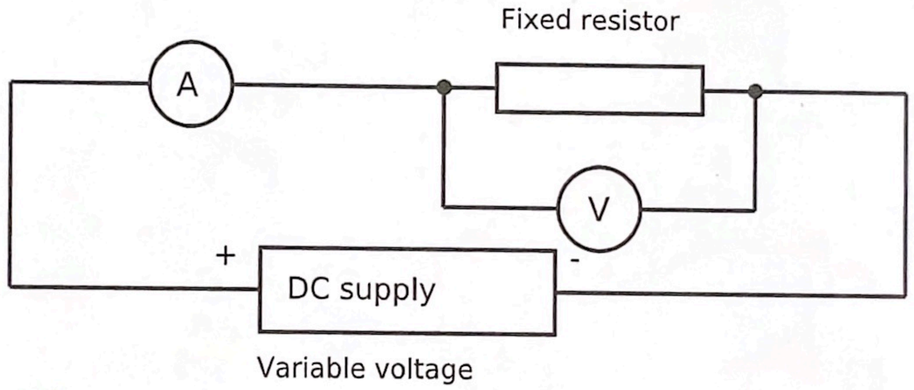

My measurements

Keep the same resistor. Rotate roles after each reading.

Trial	Voltage across resistor (V)	Current through resistor (A)
1	-10.59	11.48
2	- 8.53	9.28
3	- 6.69	7.38
4	- 4.87	5.48
5	- 3.30	3.81

My conclusion

As voltage increased, current _____.

Evidence from my readings:

_____

My results support / partly support / differ from my prediction. Circle one.

Voltage and current investigation

Name [redacted] Class _____ Date 28/10/26

How do changing voltage affect current?

My prediction

I think

that it ~~doesn't~~ make much of a difference

because

Circuit

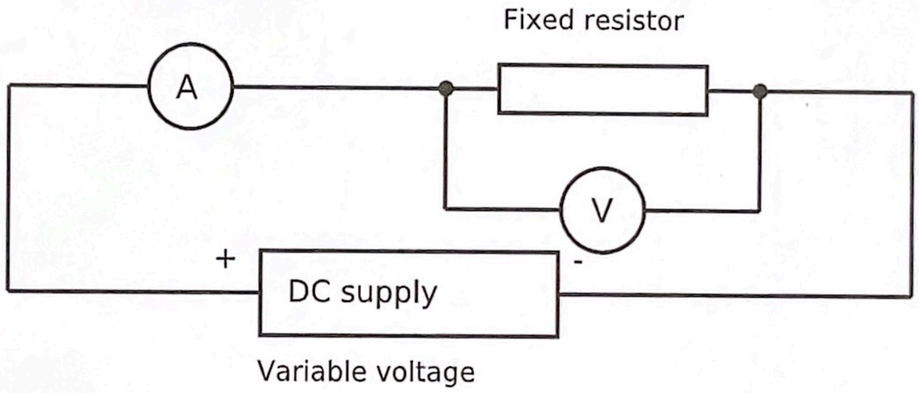

My measurements

Keep the same resistor. Rotate roles after each reading.

Trial	Voltage across resistor (V)	Current through resistor (A)
1	-10.54	11.48
2	-8.53	9.29
3	-6.~~70~~	7.37
4	-4.91	5.47
5	-3.31	3.81

My conclusion

As voltage increased, current also increased.

Evidence from my readings:

My results support / partly support / differ from my prediction. Circle one.

Voltage and current investigation

Nam[redacted] Class Science Date 28/10/26

How does changing voltage affect current?

My prediction

I think that the Stronger the voltage the More current

because because the more energy you Put in the Stronger it is

Circuit

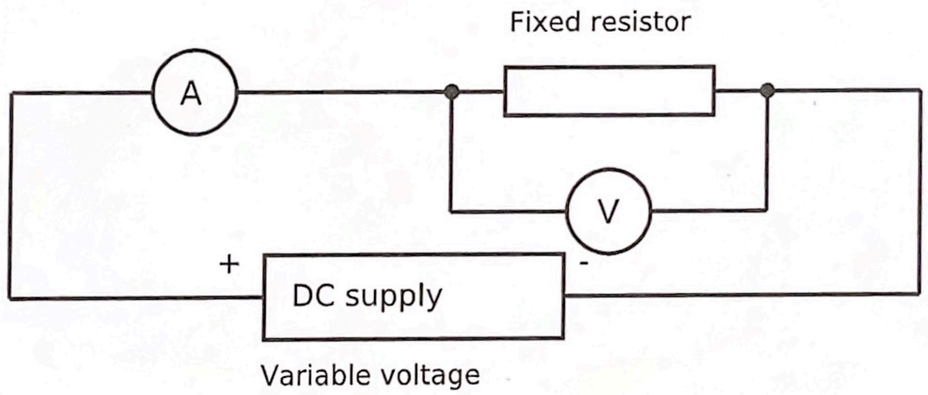

My measurements

Keep the same resistor. Rotate roles after each reading.

Trial	Voltage across resistor (V)	Current through resistor (A)
1	10.8	39.6
2	8.6	30.9
3	6.6	24.2
4	3	10.1
5	12.8	47.8

My conclusion

As voltage increased, current increased.

Evidence from my readings:

Whenever we increased the voltage the current would also increse

My results support / partly support / differ from my prediction. Circle one.

Voltage and current investigation

Name [redacted] Class _____ Date 28/10/26

How does changing voltage affect current?

My prediction

I think
it will do nothing or maybe a 1sec delay

because
I say so

Circuit

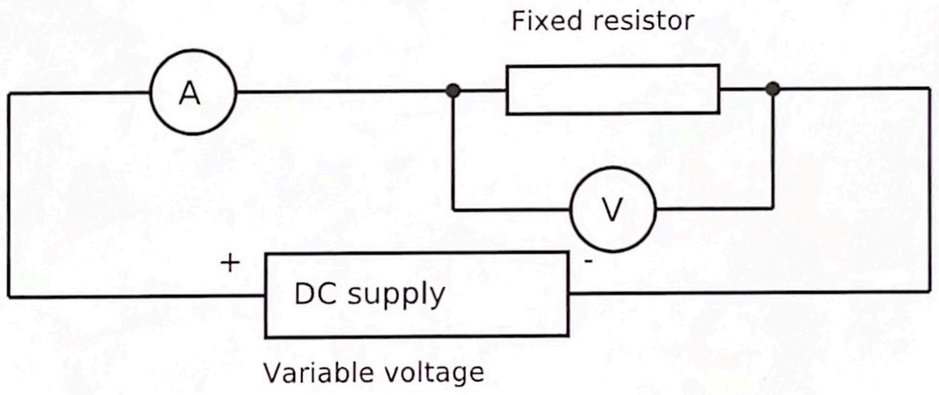

My measurements

Keep the same resistor. Rotate roles after each reading.

Trial	Voltage across resistor (V)	Current through resistor (A)
1	-10.61	11.48
2	-8.53	9.29
3	6.68	7.38
4	4.91	5.47
5	3.33	3.81

My conclusion

As voltage increased, current it went increased current.

Evidence from my readings:

whenever we increased the voltage the current would also increase

My results support / partly support / differ from my prediction. Circle one.

Voltage and current investigation

Name [redacted] Class _____ Date 28.10.26

How does changing voltage affect current?

My prediction

I think it wont make a diffence

because i just dont think it will, its just a gut feeling.

Circuit

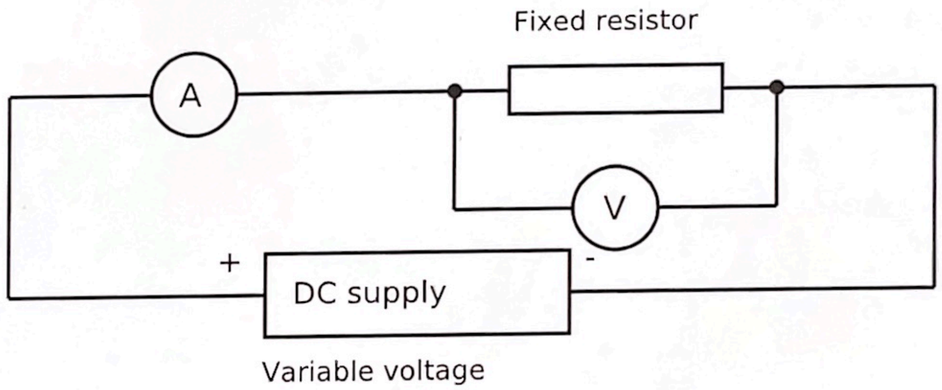

My measurements

Keep the same resistor. Rotate roles after each reading.

Trial	Voltage across resistor (V)	Current through resistor (A)
1	7.93	6.3
2	5.68	5.37
3	4.55	4.50
4	3.52	3.38
5	4.7	2.34

My conclusion

As voltage increased, current it decreases.

Evidence from my readings:

it shows on the table

My results support / partly support / differ from my prediction. Circle one.