Voltage and current investigation

Name _____ Class _____ Date _____

How does changing voltage affect current?

My prediction

I think

_____

because

_____

Circuit

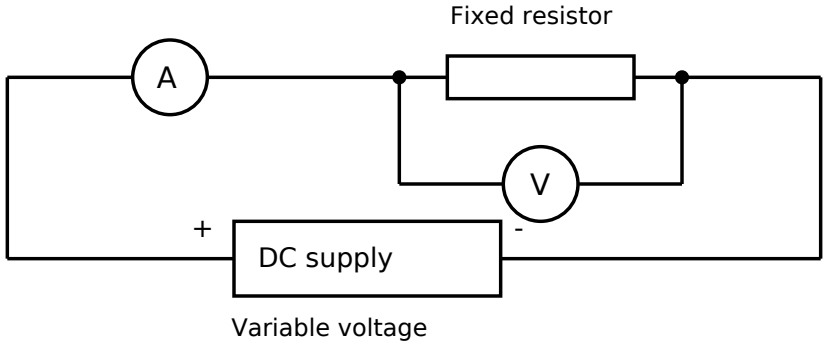

My measurements

Keep the same resistor. Rotate roles after each reading.

Trial	Voltage across resistor (V)	Current through resistor (A)
1		
2		
3		
4		
5		

My conclusion

As voltage increased, current _____.

Evidence from my readings:

_____

My results support / partly support / differ from my prediction. Circle one.

My graph and exit check

Horizontal: current (unit from meter). Vertical: voltage (V).
Start scales at zero, label axes, plot crosses and draw a best-fit line or curve.

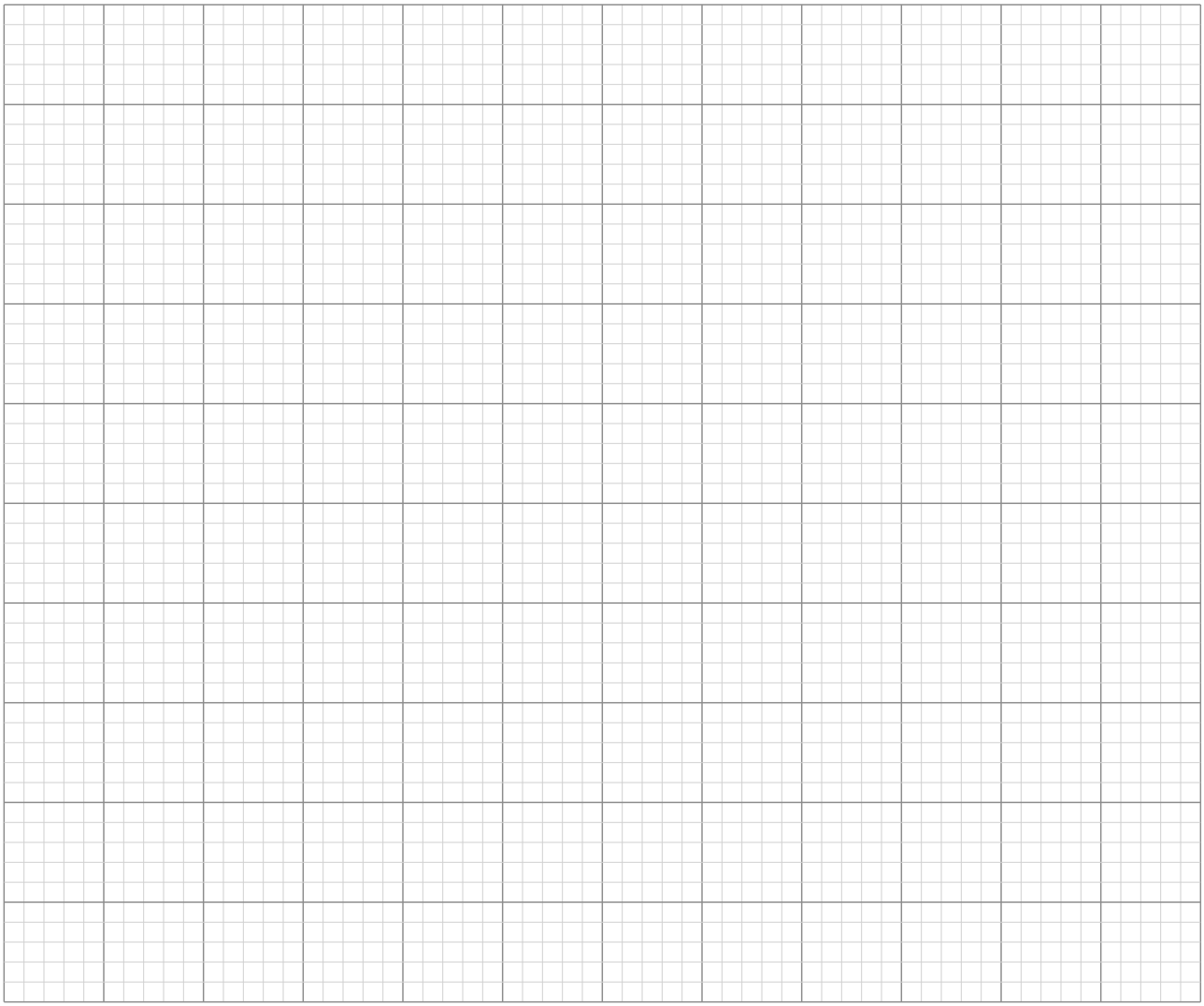

For two non-zero readings, calculate V / I: _____ and _____

What do you notice? _____

Exit check

1. Name the meter connected across the resistor. _____

2. What did you keep the same during the investigation?

---

3. State one finding supported by your data.