
Lesson 08: Parallel lamps

Parallel-circuit practical | 12 V AC

Name [redacted] Class: _____ Date: _____

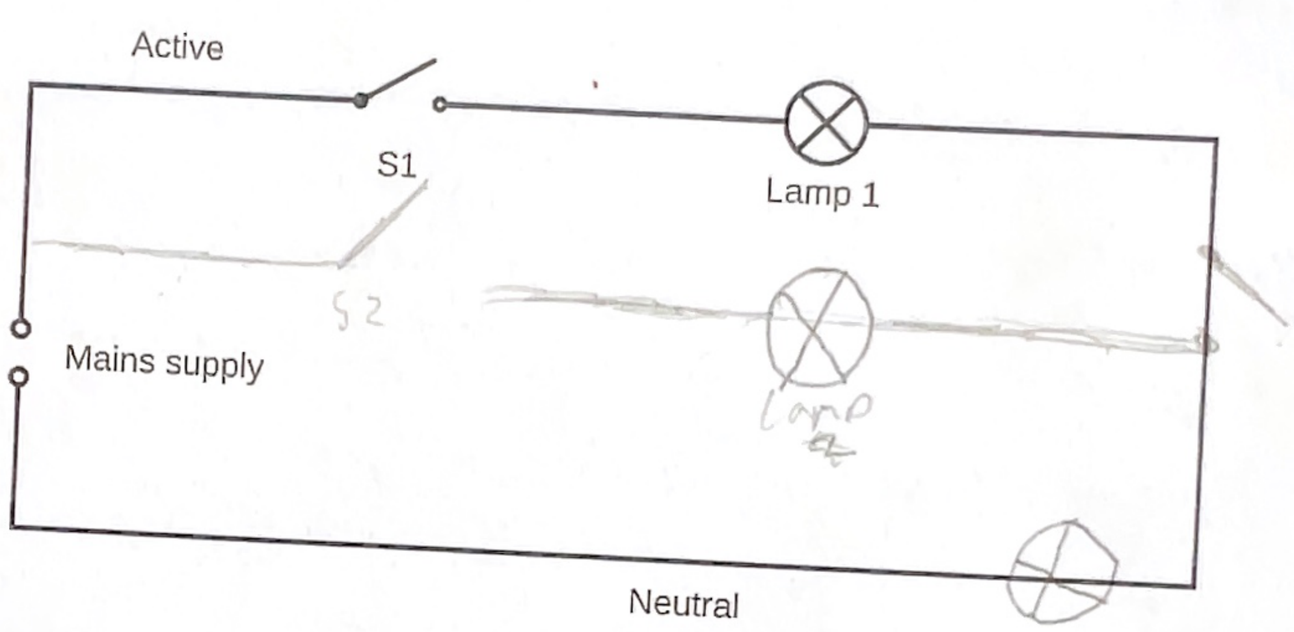1. Do now: Retrieval (5 minutes)

Modify the circuit below by adding a second lamp and a second switch. Each switch should control only its own lamp.



Build and change circuits with the supply disconnected. Ask for a teacher check before testing.

2. Build two independently switched lamps

Use your circuit drawing from Question 1. Ask your teacher to check it before building. Construct the circuit using the separate switches and two 12 V AC lamps. Take turns making and checking connections.

Switch 1	Switch 2	Lamp 1	Lamp 2
Open	Open		
Closed	Open		
Open	Closed		
Closed	Closed		

Does S1 change Lamp 2's state? no

Does S2 change Lamp 1's state? no


Lesson 08: Parallel lamps

Parallel-circuit practical | 12 V AC

Name: [redacted] Class: Science Date: 6/11/26

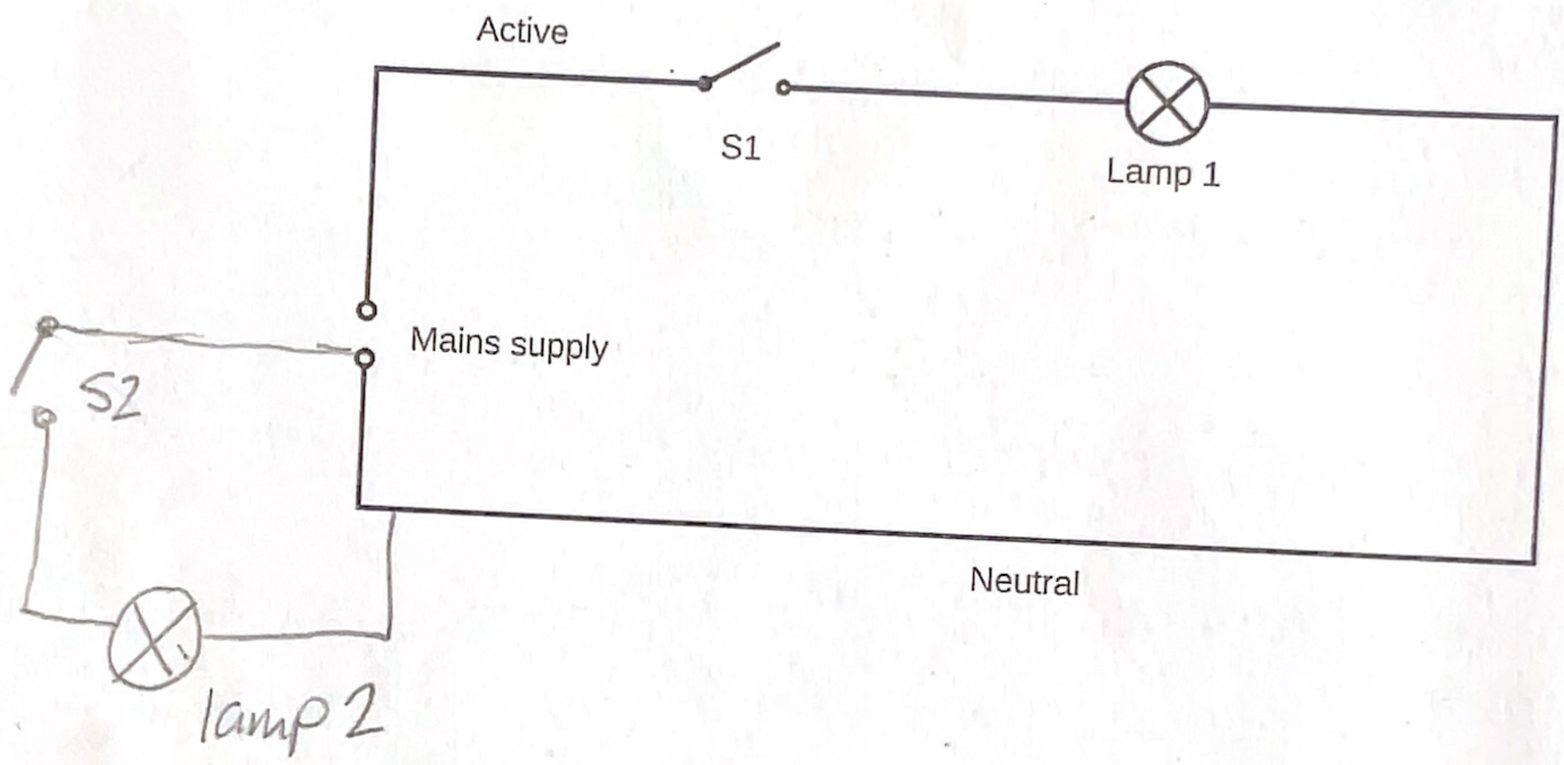1. Do now: Retrieval (5 minutes)

Modify the circuit below by adding a second lamp and a second switch. Each switch should control only its own lamp.



Build and change circuits with the supply disconnected. Ask for a teacher check before testing.

2. Build two independently switched lamps

Use your circuit drawing from Question 1. Ask your teacher to check it before building. Construct the circuit using the separate switches and two 12 V AC lamps. Take turns making and checking connections.

Switch 1	Switch 2	Lamp 1	Lamp 2
Open	Open	on	on
Closed	Open	off	on
Open	Closed	on	off
Closed	Closed	off	off

Does S1 change Lamp 2's state? No

Does S2 change Lamp 1's state? No


Lesson 08: Parallel lamps

Parallel-circuit practical | 12 V AC

Name: [redacted] Class: 10A Date: 6/11/

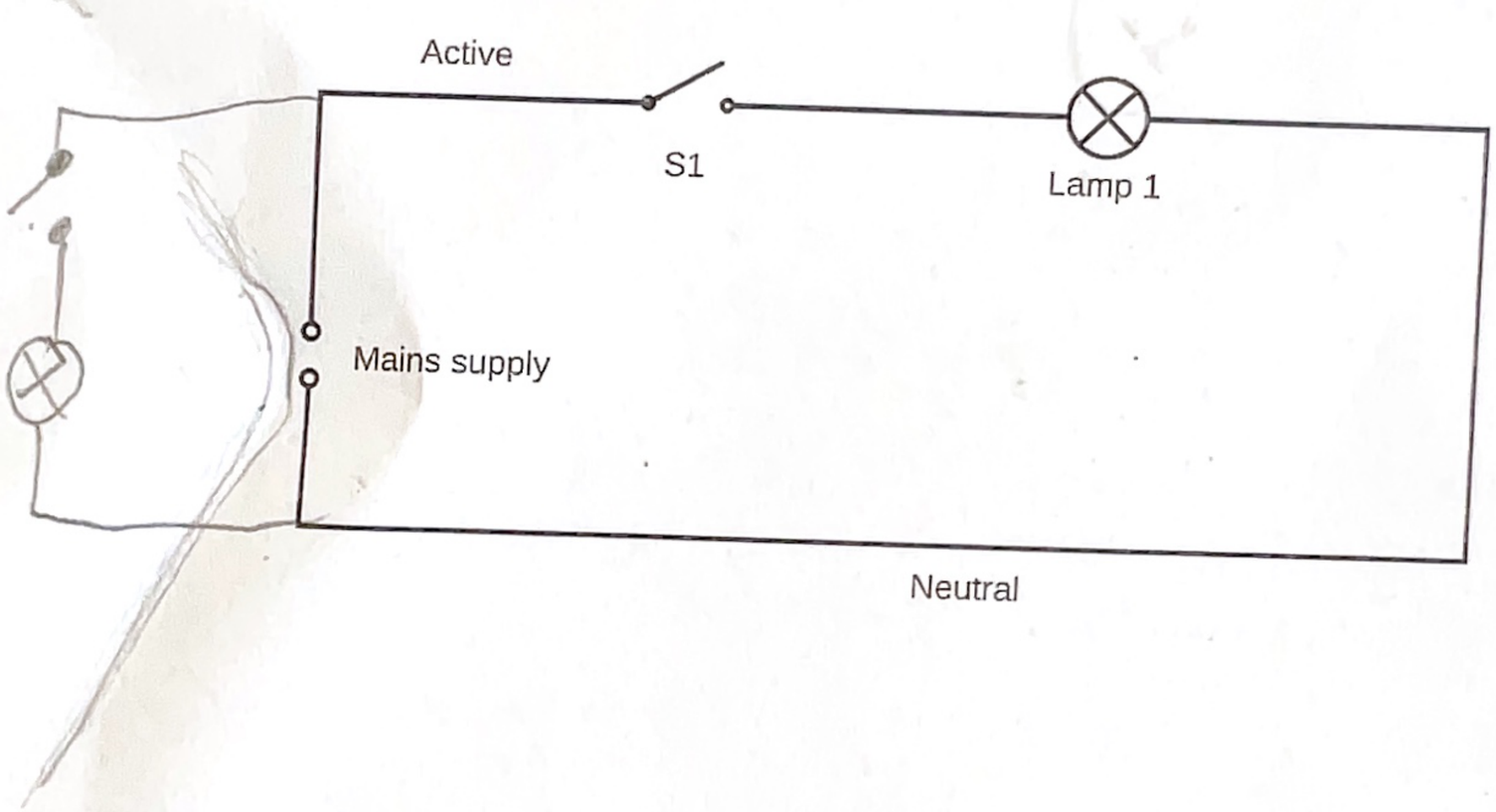1. Do now: Retrieval (5 minutes)

Modify the circuit below by adding a second lamp and a second switch. Each switch should control only its own lamp.



Build and change circuits with the supply disconnected. Ask for a teacher check before testing.

2. Build two independently switched lamps

Use your circuit drawing from Question 1. Ask your teacher to check it before building. Construct the circuit using the separate switches and two 12 V AC lamps. Take turns making and checking connections.

Switch 1	Switch 2	Lamp 1	Lamp 2
Open	Open	on	on
Closed	Open	off	on
Open	Closed	on	off
Closed	Closed	off	off

Does S1 change Lamp 2's state? no

Does S2 change Lamp 1's state? no


Lesson 08: Parallel lamps

Parallel-circuit practical – 12 V AC

Name: [redacted] Class: _____ Date: _____

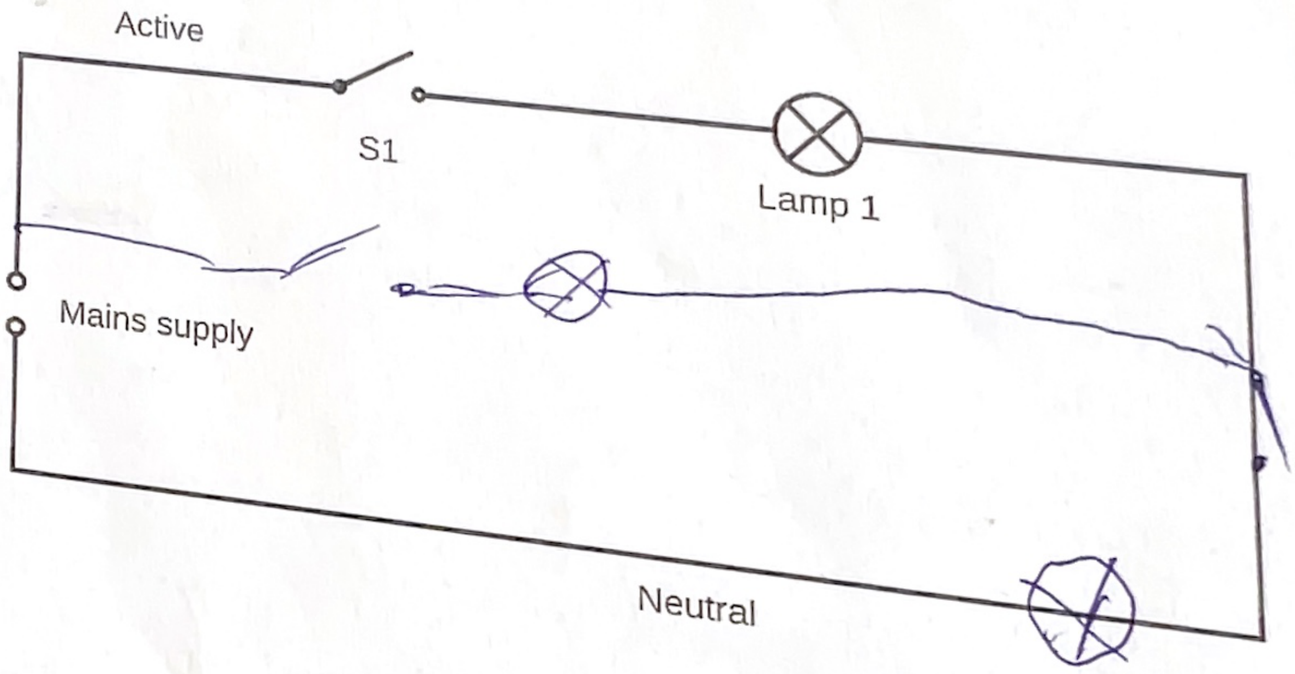1. Do now: Retrieval (5 minutes)

Modify the circuit below by adding a second lamp and a second switch. Each switch should control only its own lamp.



Build and change circuits with the supply disconnected. Ask for a teacher check before testing.

2. Build two independently switched lamps

Use your circuit drawing from Question 1. Ask your teacher to check it before building. Construct the circuit using the separate switches and two 12 V AC lamps. Take turns making and checking connections.

Switch 1	Switch 2	Lamp 1	Lamp 2
Open	Open		
Closed	Open		
Open	Closed		
Closed	Closed		

Does S1 change Lamp 2's state? no

Does S2 change Lamp 1's state? no


Lesson 08: Parallel lamps

Parallel circuit [redacted] 12 V AC

Name: [redacted] Class: 10A Date: 6/11/26

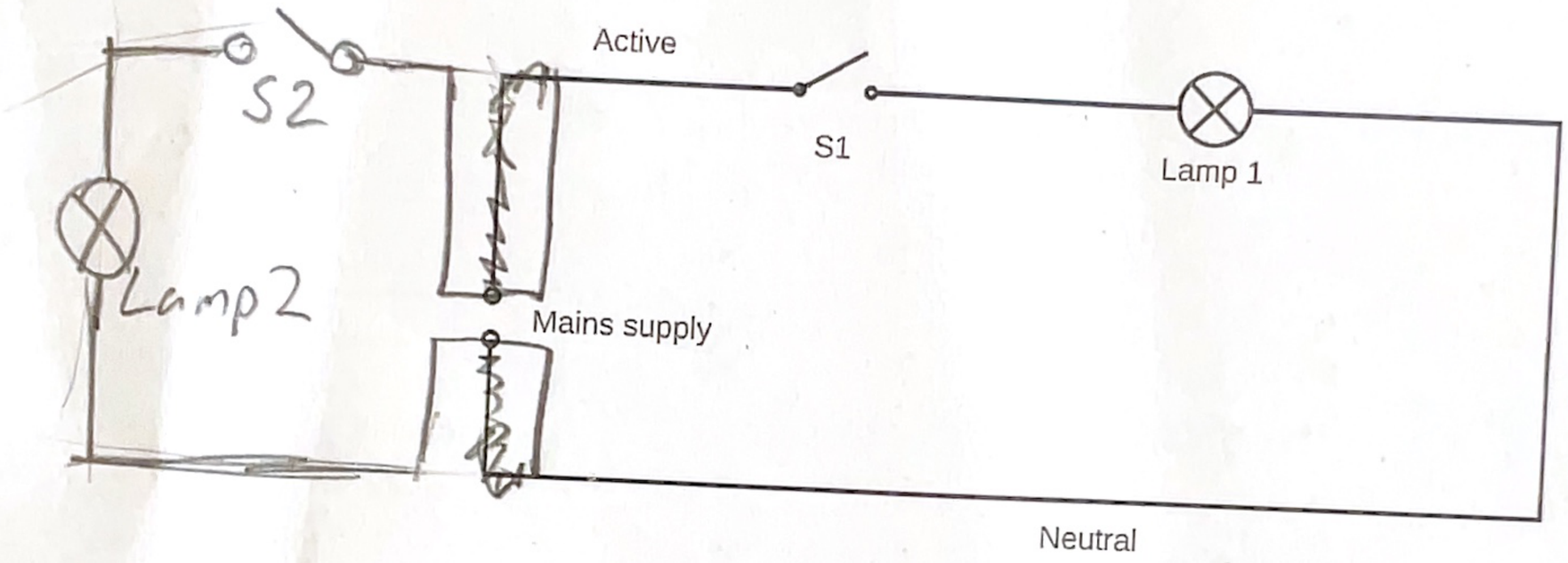1. Do now: Retrieval (5 minutes)

Modify the circuit below by adding a second lamp and a second switch. Each switch should control only its own lamp.



Build and change circuits with the supply disconnected. Ask for a teacher check before testing.

2. Build two independently switched lamps

Use your circuit drawing from Question 1. Ask your teacher to check it before building. Construct the circuit using the separate switches and two 12 V AC lamps. Take turns making and checking connections.

Switch 1	Switch 2	Lamp 1	Lamp 2
Open	Open	On	On
Closed	Open	Off	On
Open	Closed	On	Off
Closed	Closed	Off	Off

Does S1 change Lamp 2's state? _____

Does S2 change Lamp 1's state? _____